

• ارتباط تبدیل لاپلاس ولتاژ و جریان المانها

○ مقاومت

$$v(t) = R i(t)$$

$$V(s) = R I(s)$$




$$Z(s) = \frac{V(s)}{I(s)} = R$$

○ سلف

$$v(t) = L \frac{di(t)}{dt}$$

$$V(s) = L(s I(s) - i(0^-))$$

$$Z(s) = \frac{V(s)}{I(s)} = sL$$

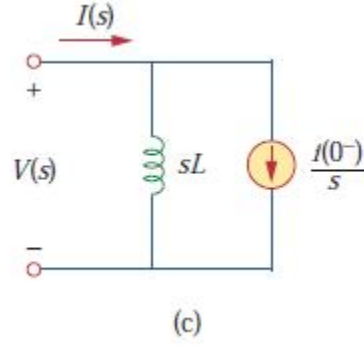
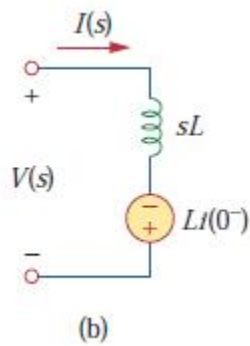
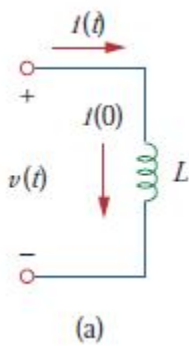


○ خازن

$$i(t) = C \frac{dv(t)}{dt}$$

$$I(s) = C(s V(s) - v(0^-))$$
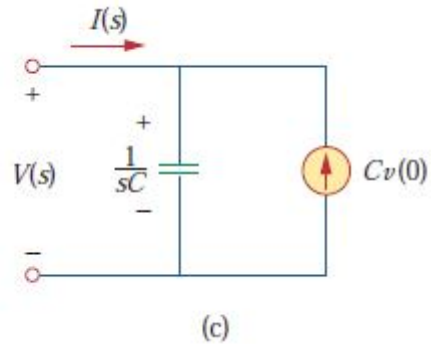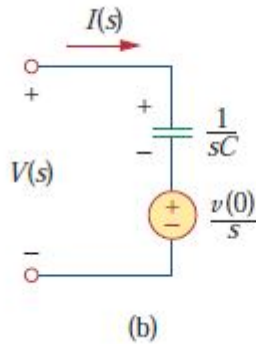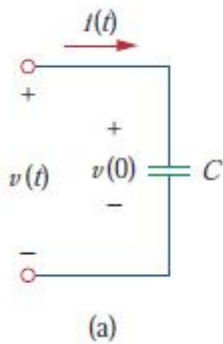
$$Z(s) = \frac{V(s)}{I(s)} = \frac{1}{sC}$$



13.3 The switch in the circuit shown has been in position a for a long time. At $t = 0$, the switch is thrown to position b.



- Find I , V_1 , and V_2 as rational functions of s .
- Find the time-domain expressions for i , v_1 , and v_2 .

Answer: (a) $I = 0.02/(s + 1250)$,
 $V_1 = 80/(s + 1250)$,
 $V_2 = 20/(s + 1250)$;

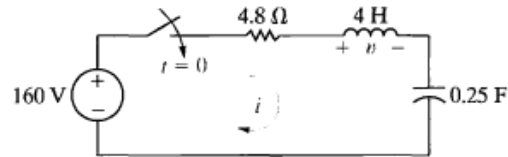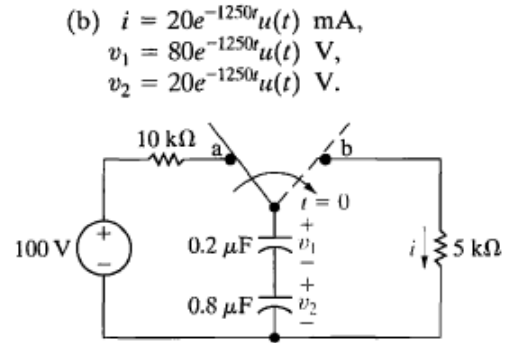13.4 The energy stored in the circuit shown is zero at the time when the switch is closed.

- Find the s -domain expression for I .
- Find the time-domain expression for i when $t > 0$.
- Find the s -domain expression for V .
- Find the time-domain expression for v when $t > 0$.

Answer: (a) $I = 40/(s^2 + 1.2s + 1)$;
 (b) $i = (50e^{-0.6t} \sin 0.8t)u(t)$ A;
 (c) $V = 160s/(s^2 + 1.2s + 1)$;
 (d) $v = [200e^{-0.6t} \cos(0.8t + 36.87^\circ)]u(t)$ V.



Determine $v_o(t)$ in the circuit of Fig. 16.6, assuming zero initial conditions.

Answer: $20(1 - e^{-2t} - 2te^{-2t})u(t)$ V.

Practice Problem 16.1

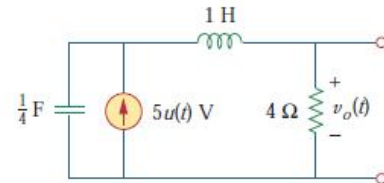


Figure 16.6
For Practice Prob. 16.1.

Find $v_o(t)$ in the circuit shown in Fig. 16.9. Note that, since the voltage input is multiplied by $u(t)$, the voltage source is a short for all $t < 0$ and $i_L(0) = 0$.

Answer: $(24e^{-2t} - 4e^{-t/3})u(t)$ V.

Practice Problem 16.2

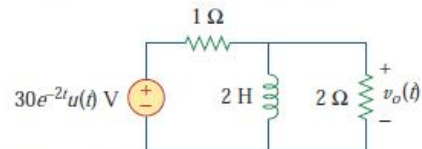


Figure 16.9
For Practice Prob. 16.2.

Practice Problem 16.3

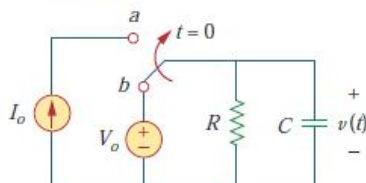


Figure 16.11
For Practice Prob. 16.3.

The switch in Fig. 16.11 has been in position b for a long time. It is moved to position a at $t = 0$. Determine $v(t)$ for $t > 0$.


Answer: $v(t) = (V_o - I_o R)e^{-t/\tau} + I_o R$, $t > 0$, where $\tau = RC$.

13.6 The initial charge on the capacitor in the circuit shown is zero.


- Find the s -domain Thévenin equivalent circuit with respect to terminals a and b.
- Find the s -domain expression for the current that the circuit delivers to a load consisting of a 1 H inductor in series with a 2 Ω resistor.

Answer: (a) $V_{Th} = V_{ab} = [20(s + 2.4)]/[s(s + 2)]$,
 $Z_{Th} = 5(s + 2.8)/(s + 2)$;

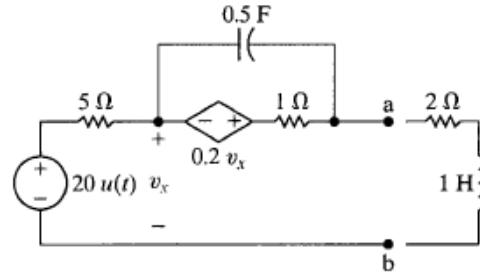(b) $I_{ab} = [20(s + 2.4)]/[s(s + 3)(s + 6)]$.



مدار تزویج

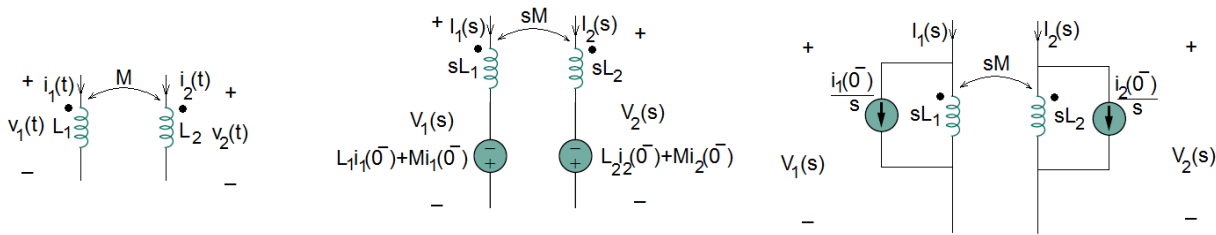

• تابع انتقال

The **transfer function** $H(s)$ is the ratio of the output response $Y(s)$ to the input excitation $X(s)$, assuming all initial conditions are zero.

$$H(s) = \frac{Y(s)}{X(s)}$$

$$H(s) = \text{Voltage gain} = \frac{V_o(s)}{V_i(s)}$$

$$H(s) = \text{Current gain} = \frac{I_o(s)}{I_i(s)}$$

$$H(s) = \text{Impedance} = \frac{V(s)}{I(s)}$$

$$H(s) = \text{Admittance} = \frac{I(s)}{V(s)}$$

○ اگر $x(t) = \delta(t)$ آنگاه $Y(s) = H(s)$. بنابراین:

$$Y(s) = H(s) \quad \text{or} \quad y(t) = h(t)$$

$$h(t) = \mathcal{L}^{-1}[H(s)]$$