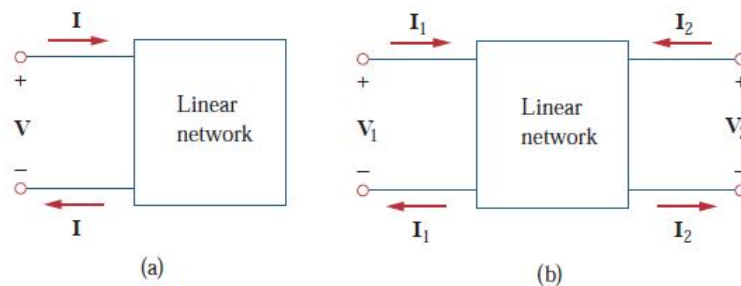


فصل 18 کتاب نیلسون، فصل 19 کتاب الکساندر

دوقطبی ها

دو قطبی ها در مقابل تک قطبی ها



• پارامترهای امپدانس

$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = [z] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{aligned} z_{11} &= \left. \frac{V_1}{I_1} \right|_{I_2=0}, & z_{12} &= \left. \frac{V_1}{I_2} \right|_{I_1=0} \\ z_{21} &= \left. \frac{V_2}{I_1} \right|_{I_2=0}, & z_{22} &= \left. \frac{V_2}{I_2} \right|_{I_1=0} \end{aligned}$$


$z_{11}$  = Open-circuit input impedance

$z_{12}$  = Open-circuit transfer impedance from port 1 to port 2

$z_{21}$  = Open-circuit transfer impedance from port 2 to port 1

$z_{22}$  = Open-circuit output impedance

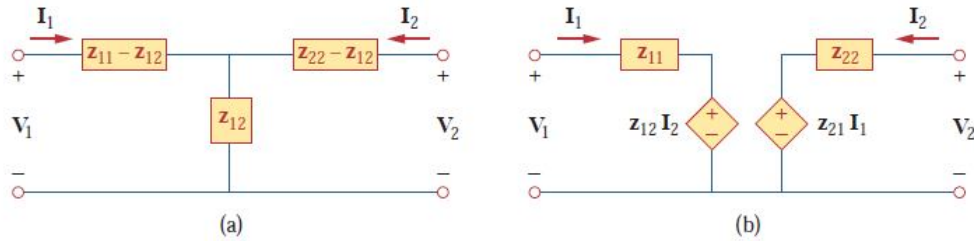
برای بعضی مدارهای دوقطبی، پارامترهای امپدانس وجود ندارد: مثلا ترانسفورماتور ایده آل



Find the  $z$  parameters of the two-port network in Fig. 19.9.

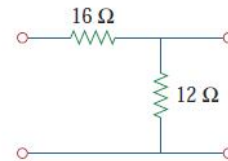
### Practice Problem 19.1

**Answer:**  $z_{11} = 28 \Omega$ ,  $z_{12} = z_{21} = z_{22} = 12 \Omega$ .


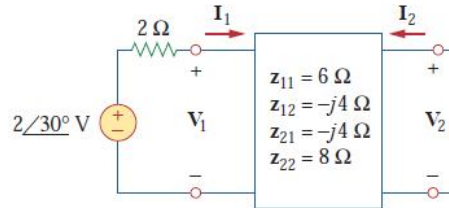
### Practice Problem 19.2

Calculate  $I_1$  and  $I_2$  in the two-port of Fig. 19.11.



• پارامترهای ادمیتانس

$$\begin{aligned} I_1 &= y_{11}V_1 + y_{12}V_2 \\ I_2 &= y_{21}V_1 + y_{22}V_2 \end{aligned}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [y] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


$$\begin{aligned} y_{11} &= \left. \frac{I_1}{V_1} \right|_{V_2=0}, & y_{12} &= \left. \frac{I_1}{V_2} \right|_{V_1=0} \\ y_{21} &= \left. \frac{I_2}{V_1} \right|_{V_2=0}, & y_{22} &= \left. \frac{I_2}{V_2} \right|_{V_1=0} \end{aligned}$$

$y_{11}$  = Short-circuit input admittance

$y_{12}$  = Short-circuit transfer admittance from port 2 to port 1

$y_{21}$  = Short-circuit transfer admittance from port 1 to port 2

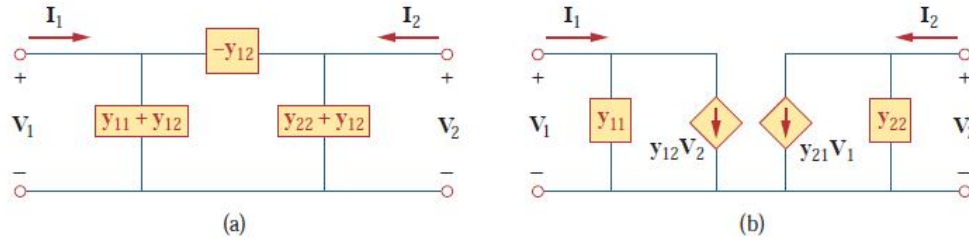
$y_{22}$  = Short-circuit output admittance



Obtain the  $y$  parameters for the  $T$  network shown in Fig. 19.16.

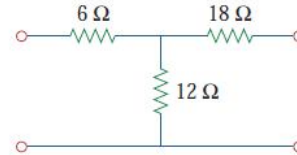
### Practice Problem 19.3

**Answer:**  $y_{11} = 75.77 \text{ mS}$ ,  $y_{12} = y_{21} = -30.3 \text{ mS}$ ,  $y_{22} = 45.47 \text{ mS}$ .


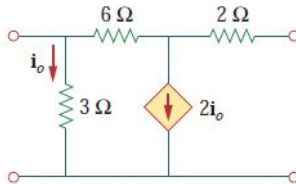
### Practice Problem 19.4

Obtain the  $y$  parameters for the circuit in Fig. 19.19.



**Answer:**  $y_{11} = 0.625 \text{ S}$ ,  $y_{12} = -0.125 \text{ S}$ ,  $y_{21} = 0.375 \text{ S}$ ,  $y_{22} = 0.125 \text{ S}$ .

• پارامترهای هیبرید (ترکیبی)

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = [h] \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$


$$\begin{aligned} h_{11} &= \left. \frac{V_1}{I_1} \right|_{V_2=0}, & h_{12} &= \left. \frac{V_1}{V_2} \right|_{I_1=0} \\ h_{21} &= \left. \frac{I_2}{I_1} \right|_{V_2=0}, & h_{22} &= \left. \frac{I_2}{V_2} \right|_{I_1=0} \end{aligned}$$

$h_{11}$  = Short-circuit input impedance

$h_{12}$  = Open-circuit reverse voltage gain

$h_{21}$  = Short-circuit forward current gain

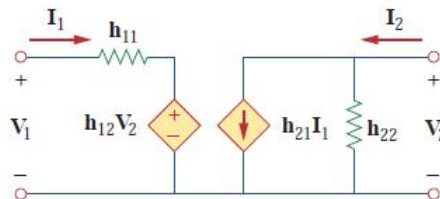$h_{22}$  = Open-circuit output admittance




• پارامترهای  $g$  (پارامترهای معکوس  $h$ )

$$\begin{aligned} I_1 &= g_{11}V_1 + g_{12}I_2 \\ V_2 &= g_{21}V_1 + g_{22}I_2 \end{aligned}$$

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = [g] \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

$$\begin{aligned} g_{11} &= \left. \frac{I_1}{V_1} \right|_{I_2=0}, & g_{12} &= \left. \frac{I_1}{I_2} \right|_{V_1=0} \\ g_{21} &= \left. \frac{V_2}{V_1} \right|_{I_2=0}, & g_{22} &= \left. \frac{V_2}{I_2} \right|_{V_1=0} \end{aligned}$$

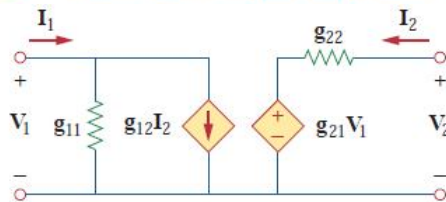
- $g_{11}$  = Open-circuit input admittance
- $g_{12}$  = Short-circuit reverse current gain
- $g_{21}$  = Open-circuit forward voltage gain
- $g_{22}$  = Short-circuit output impedance



Determine the  $h$  parameters for the circuit in Fig. 19.24.


**Answer:**  $h_{11} = 2.4 \Omega$ ,  $h_{12} = 0.4$ ,  $h_{21} = -0.4$ ,  $h_{22} = 200 \text{ mS}$ .

### Practice Problem 19.5

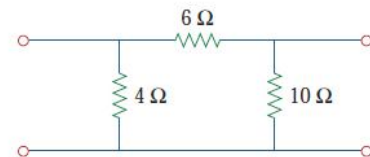
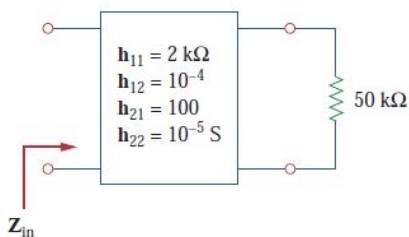
### Practice Problem 19.6

Find the impedance at the input port of the circuit in Fig. 19.27.




**Answer:**  $1.6667 \text{ k}\Omega$ .

For the ladder network in Fig. 19.30, determine the  $g$  parameters in the  $s$  domain.

**Answer:**  $[g] = \begin{bmatrix} \frac{s+2}{s^2+3s+1} & -\frac{1}{s^2+3s+1} \\ \frac{1}{s^2+3s+1} & \frac{s(s+2)}{s^2+3s+1} \end{bmatrix}$ .

**Practice Problem 19.7**

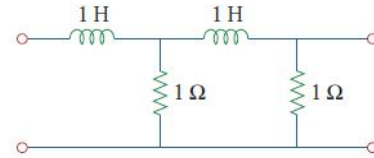

**Figure 19.30**  
For Practice Prob. 19.7.

• پارمترهای  $t$

$$\begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = [T] \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$


$$\begin{aligned} A &= \left. \frac{V_1}{V_2} \right|_{I_2=0}, & B &= -\left. \frac{V_1}{I_2} \right|_{V_2=0} \\ C &= \left. \frac{I_1}{V_2} \right|_{I_2=0}, & D &= -\left. \frac{I_1}{I_2} \right|_{V_2=0} \end{aligned}$$

- A** = Open-circuit voltage ratio
- B** = Negative short-circuit transfer impedance
- C** = Open-circuit transfer admittance
- D** = Negative short-circuit current ratio

Find  $I_1$  and  $I_2$  if the transmission parameters for the two-port in Fig. 19.36 are

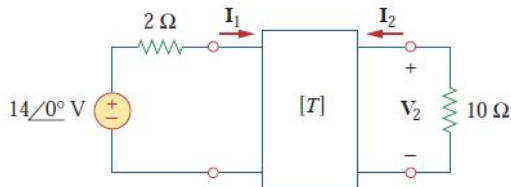**Practice Problem 19.9**

$$\begin{bmatrix} 5 & 10 \Omega \\ 0.4 \text{ S} & 1 \end{bmatrix}$$




• ارتباط بین پارامترها

Find the  $z$  parameters of the op amp circuit in Fig. 19.38. Show that the circuit has no  $y$  parameters.

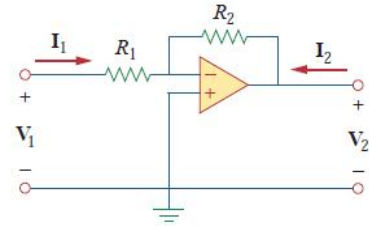
**Practice Problem 19.11**

**Answer:**  $[z] = \begin{bmatrix} R_1 & 0 \\ -R_2 & 0 \end{bmatrix}$ . Since  $[z]^{-1}$  does not exist,  $[y]$  does not exist.




• اتصال شبکه‌ها

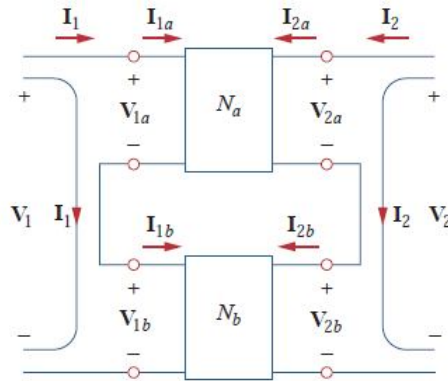○ اتصال سری: با استفاده از پارامترهای  $Z$




$$[z] = [z_a] + [z_b]$$

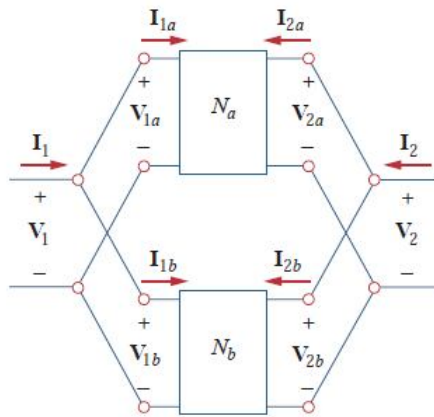○ اتصال موازی: با استفاده از پارامترهای  $y$



$$[y] = [y_a] + [y_b]$$

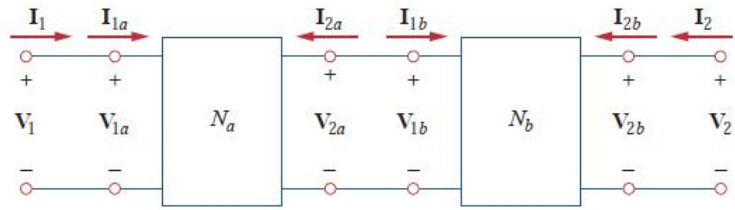○ اتصال آبشاری: با استفاده از پارامترهای  $t$



$$[\mathbf{T}] = [\mathbf{T}_a][\mathbf{T}_b]$$